

# **1007ICT / 1807ICT / 7611ICT**

## **Computer Systems & Networks**

Assignment Project Exam Help

<https://powcoder.com>

### **3A. Digital Logic and Digital Circuits**

Add WeChat powcoder

Dr. Sven Venema

Dr. Vallipuram Muthukkumarasamy

---

# Last Section: Data Representation

## Topics Covered:

- Representing binary integers
- Conversion from binary to decimal
- Hexadecimal and octal representations
- Binary number operations
- One's complement and two's complement
- Representing characters, images and audio

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Lecture Content

- Learning objectives
- **Digital logic**, Basic logic gates, Boolean algebra
- Combinatorial logic gates

**Assignment Project Exam Help**

**<https://powcoder.com>**

**Add WeChat powcoder**

# Learning Objectives

At the end of this lecture you will have:

- Gained an understanding of basic logic gates
- Learnt the truth tables associated with the basic logic gates
- Gained an understanding of combinatorial logic gates
- Learnt the truth tables associated with combinatorial logic gates

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Digital Logic (Section 2.2)

- All digital computers are built from a set of low level digital logic switches or **Logic Gates**.
- Gates operate on binary signals that only have one of two values:
  - Signals from 0 to 2 volts is used to represent a binary 0 (**OFF**)
  - Signals from 3 to 5 volts is used to represent a binary 1 (**ON**)
  - Signals between 2 and 3 volts represent an invalid state
- Three basic logic functions that can be applied to binary signals:
  - AND: output true if ALL inputs are true
  - OR: output true if ANY input is true
  - NOT: output is the inverse of the input
- More complex functions can be built from these three basic gates

# Basic Logic Gates (Section 2.4)



**Name**

**AND**

**OR**

**NOT**

**Symbol**

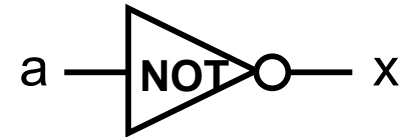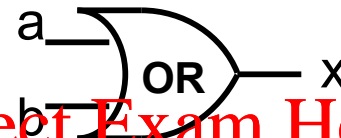

**Boolean expression**

$$x = a \text{ AND } b$$

$$x = a \text{ OR } b$$

$$x = \overline{a}$$

**Truth Table**

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

A	X
0	1
1	0

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Boolean Algebra


- There is a basic set of rules about combining simple binary functions.

**OR**

- $x \text{ OR } 0 = x$
- $x \text{ OR } 1 = 1$
- $x \text{ OR } x = x$
- $x \text{ OR } \overline{x} = 1$
- $\overline{(\overline{x})} = x$

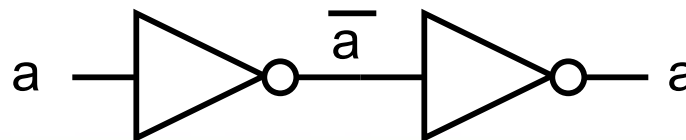**AND**

- $x \text{ AND } 0 = 0$
- $x \text{ AND } 1 = x$
- $x \text{ AND } x = x$
- $x \text{ AND } \overline{x} = 0$





# Combinatorial Logic Gates

**Name**

**NAND**


**NOR**

**XOR**

**Symbol**



**Equivalent**

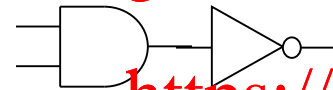

Next Slide

**Boolean expression**

$$x = a \text{ AND } b$$

$$x = a \text{ OR } b$$

$$x = a \text{ XOR } b$$

**Truth Table**

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0



# Boolean Algebra - 2

- This second set of rules are more powerful.

**OR** - form

**AND** - form

$$\overline{(x \text{ OR } y)} = \bar{x} \text{ AND } \bar{y}$$



$$\overline{(x \text{ AND } y)} = \bar{x} \text{ OR } \bar{y}$$

<https://powcoder.com>

Add WeChat powcoder

**OR** - form

**AND** - form

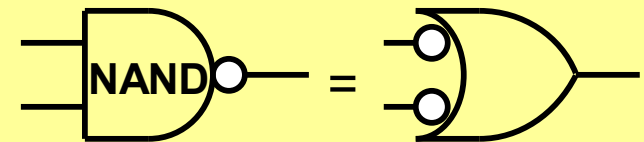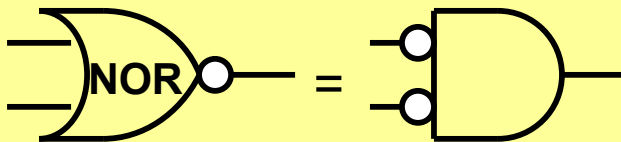

**DeMorgan's Theorem**

# The eXclusive-OR Gate (XOR)




A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

- Looking at the truth table we see that the XOR function can be described as:


- $$x = (a \text{ AND } \bar{b}) \text{ OR } (\bar{a} \text{ AND } b)$$
- $$x = a \text{ XOR } b$$

- <https://powcoder.com>
- This function can be built in 3 ways:


Add WeChat powcoder Demorgan's Theorem

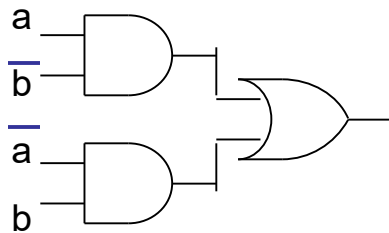
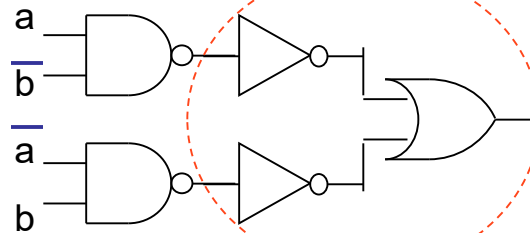
$$x = (a \text{ AND } \bar{b}) \text{ OR } (\bar{a} \text{ AND } b)$$



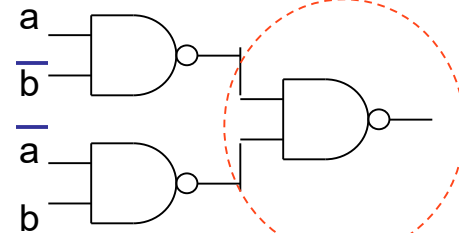
$$x = (a \text{ AND } \bar{b}) \text{ OR } (\bar{a} \text{ AND } b)$$





$$x = (a \text{ AND } b) \text{ AND } (\bar{a} \text{ AND } b)$$


4011  
Quad NAND gate

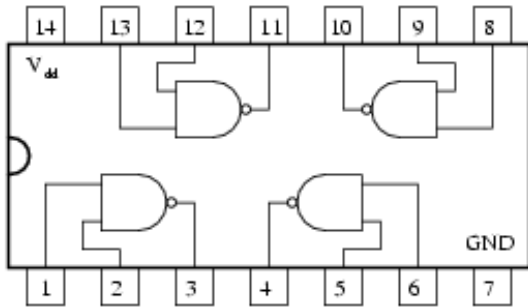


4001  
Quad NOR gate

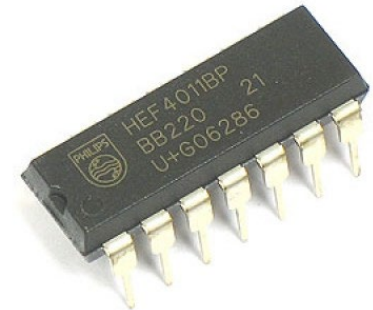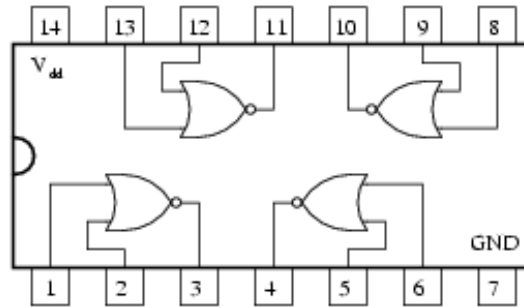

4081  
Quad AND gate

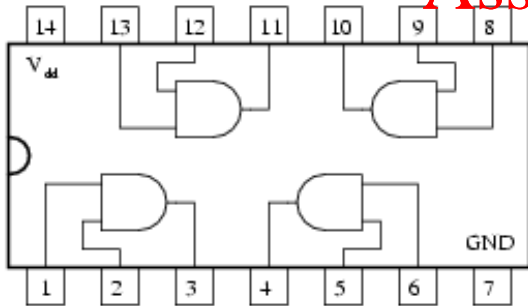

4071  
Quad OR gate

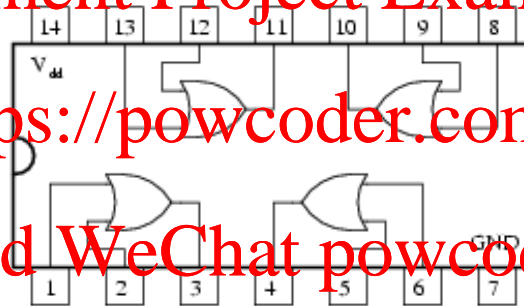


Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder



4070  
Quad XOR gate

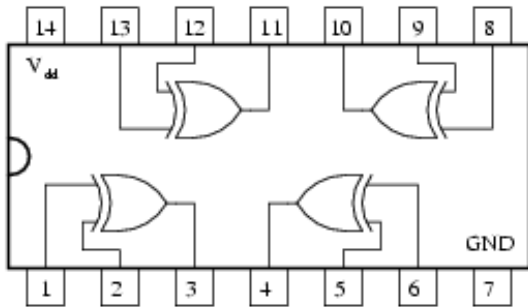

4069  
Hex inverter

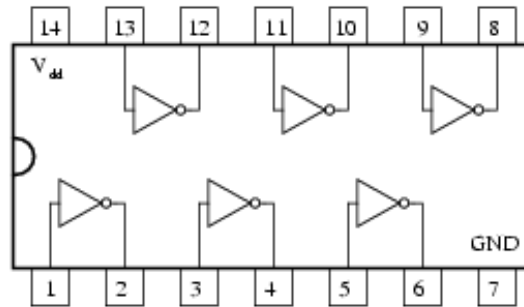


# Logic Unit

- Let's try to create a “programmable” logic unit that permits us to apply a predefined logic function to a given set of inputs.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

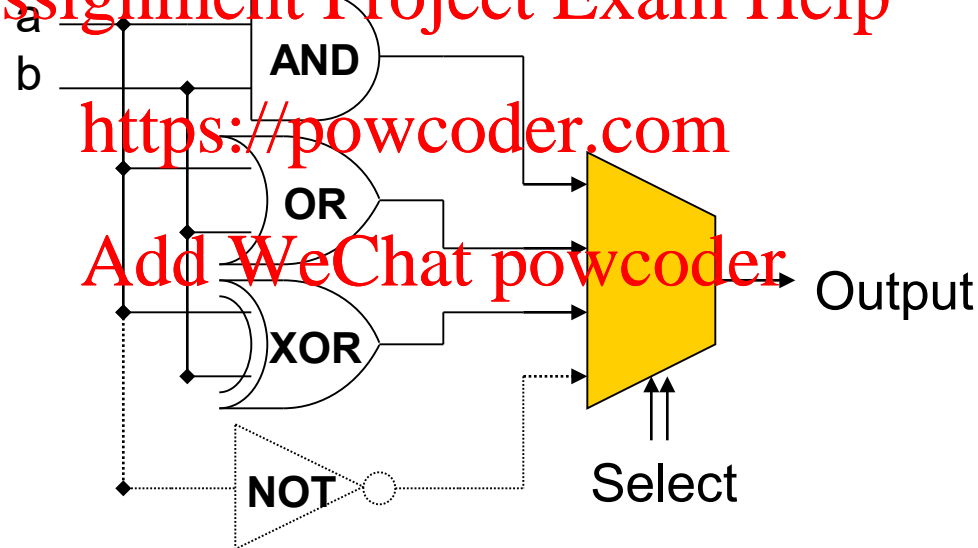

- We need a function that lets us select what operation to perform

# Summary

Have considered:

- Operation of basic logic gates
- Combinatorial logic gates, Truth tables

**Assignment Project Exam Help**

**<https://powcoder.com>**

**Add WeChat powcoder**

# Next....

- Logic unit, Selection logic, Decoder logic <https://powcoder.com>
- Multiplexing and demultiplexing [Add WeChat powcoder](https://powcoder.com)